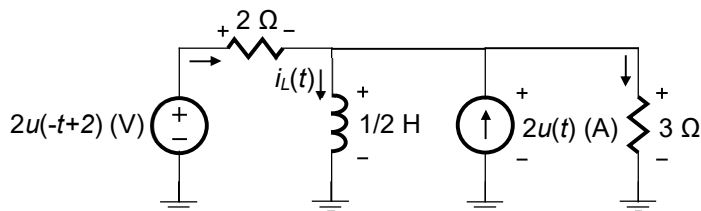




First Test, Circuits III, August 29, 2023, Danilo Rairán

Name: _____ Code: _____

1. a) compute the o.d.e for i_L , using symbols instead of numerical values.
Use superposition. (0.5/2.5)
 Compute and plot the following equations (you can use the synthetic form):
 - b) natural responses, (0.8/2.5)
 - c) forced responses, (0.7/2.5)
 - d) complete response. (0.5/2.5)



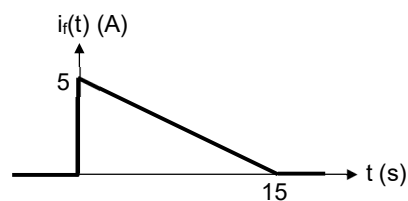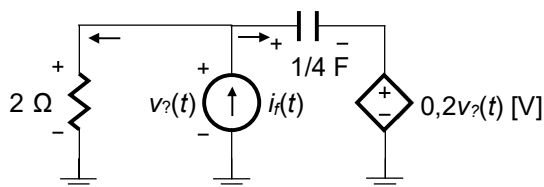2. a) Compute an o.d.e for $v_2(i_f)$ using symbols instead of numerical values. (0.5/2.5)
 Compute and plot the following equations:
 - b) natural responses. (0.8/2.5)
 - c) forced response. (0.7/2.5)
 - d) complete response. (0.5/2.5)



3. **Bonus 1:** How would you mathematically prove that one of your complete answers is correct?
Bonus 2: Apply that mathematical proof to one of the exercises.


Name: _____ Code: _____

= last digit of your code + 1.

1. **Compute and plot** the natural, forced and complete responses for the voltage in the capacitor, $v_C(t)$.

$$R = 1 + \#/10 \text{ } (\Omega)$$

i_R is the current through R .


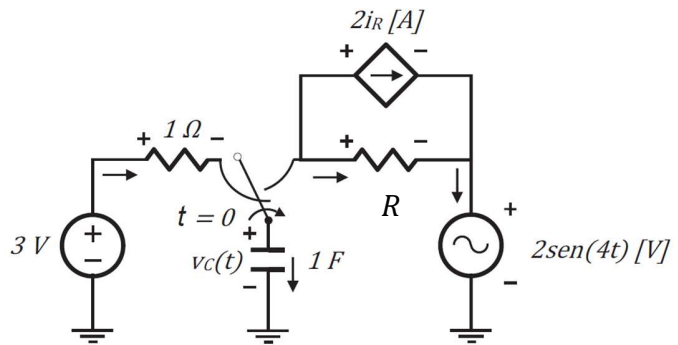


2. Using Laplace Transform, **compute and plot** the zir , zsr and complete response for the voltage in the capacitor, $v_C(t)$.

Assume $v_C(0) = 1 \text{ V}$.

$$t_0 = (1 + \#/10)\tau \text{ (s)}$$

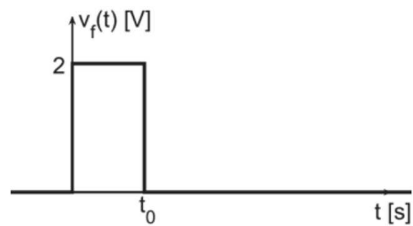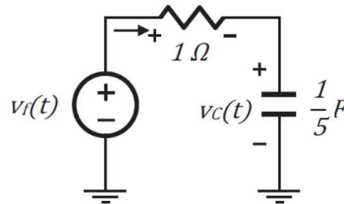In addition, show that the answer satisfies the **ode**.



1. 2.5

2. 2.5